

# Digital Design (DD) Exercise 3

7 segment Display – Single Digit

Christoph Riedl





# 7 Segment Display – Single Digit

Basic – Team Task



## TASK DESCRIPTION




#### Qualitatively

- If the CPU Reset button is pressed, all digits of the 7 segment display are switched OFF.
- If the switch SW(15) is switched ON, the  $digit_{place}$  digit show the number  $digit_{number}$

#### **Quantitatively:**

The  $digit_{place}$  can be calculated as follows  $digit_{place} = abs(Team\ number\ -2)$ 

 $digit_{place}$  position:

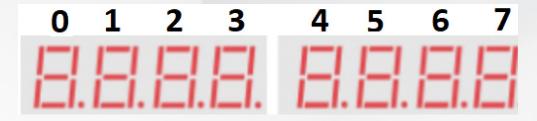

The  $digit_{number}$  is the team number






# **ARCHITECTURE COMPONENTS**



S7segm\_top.vhd → top level

S7segm.vhd → Block is used to generate the proper anode an cathode signals for the dedicated digits of the 7 segment display

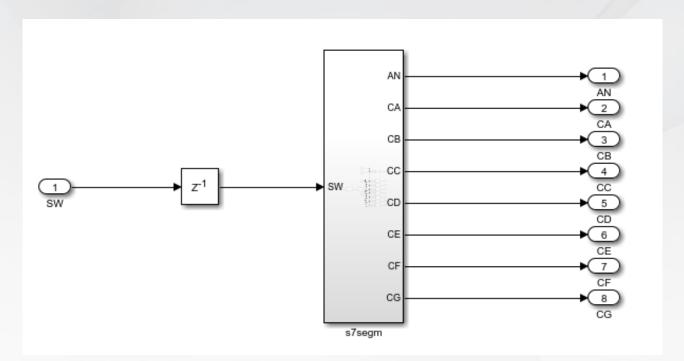
https://digilent.com/reference/programmable-logic/nexys-4-ddr/reference-manual





# **USEFUL BLOCKS**




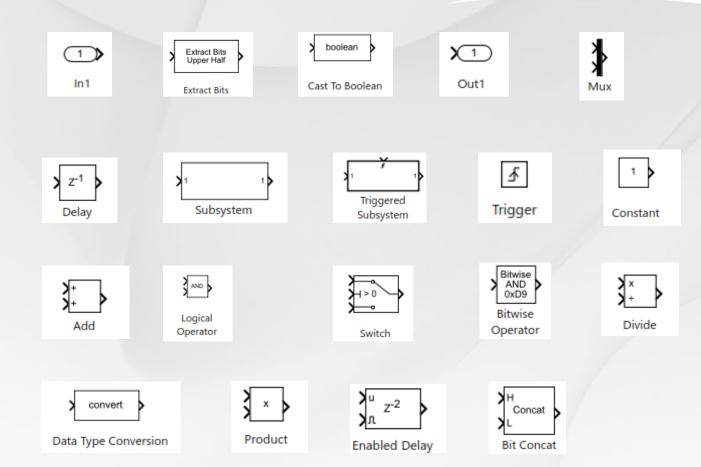



# ANODE CATHODE CONTD.



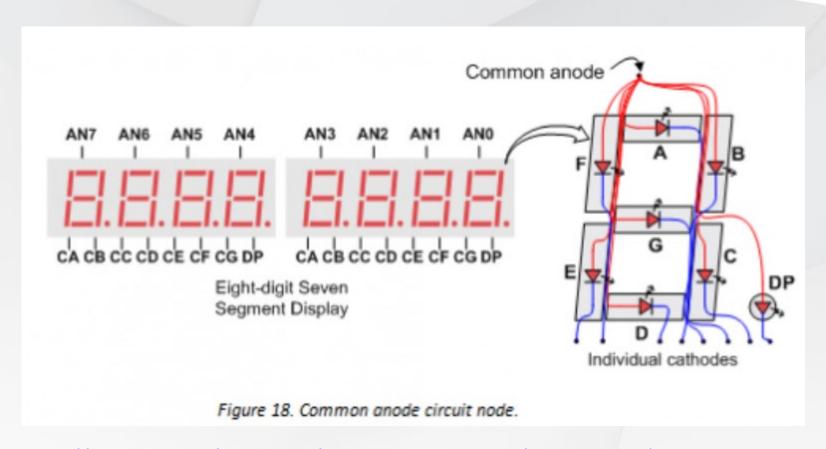

https://digilent.com/reference/programmable-logic/nexys-4-ddr/reference-manual



### **DELIVERABLES**



- Send the codable Simulink graphic (\*.slx) in a zipped file in a "graph" folder
- Add a small video (mp4) "7segm\_single\_dig\_basic\_video" to the zip file in a "video" folder to demonstrate the right behavior
  - To compress a HQ video from your mobile phone, you could use a tool for video compression:
  - E.g.: <a href="https://video-verkleinern.online-umwandeln.de/">https://video-verkleinern.online-umwandeln.de/</a>

